



This circuit leaves two NANDs unused, though they don't have to be these two.

Experiment:

- \* If you're getting a lot of noise, they may be inadvertently toggling. Ground their inputs to prevent that.
- \* Use one to make another pitch oscillator like in Stage 2, then combine their outputs with 10k "mixing" resistors. Point it at a different part of the LED string. Does it sound cool?!

tommy@oskitone.com

Sheet: /light\_theremin\_sequencer/

File: light\_theremin\_sequencer.kicad\_sch

**Title: Light theremin sequencer**

Size: A4 Date: Aug '23

KiCad E.D.A. kicad (6.0.1-0)

Rev:

Id: 9/10